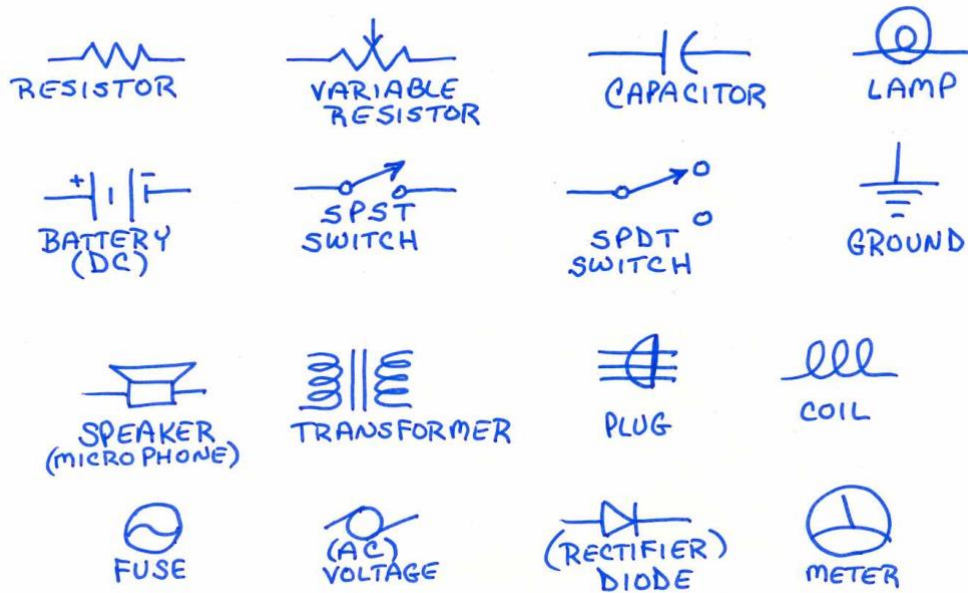


CIRCUIT SYMBOLS



Using the Circuit Symbols above, make your own circuits.

A TWO-BATTERY FLASHLIGHT.

FOUR LIGHTS THAT ALL GO OUT
IF ONE GOES OUT.

FOUR LIGHTS IN YOUR
BEDROOM.

THE BATTERY, HEADPHONES,
AND VOLUME CONTROL OF A
MUSIC DEVICE.

Using the Circuit Symbols above, make your own circuits.

A 120V AC-3V DC STEP-DOWN
TRANSFORMER

A CAPACITOR, METER, & LAMP
ON A SURGE PROTECTOR

A CELL PHONE

A BAND: 3 MICS, 2 GUITARS, 1
AMP, 2 SPEAKERS

A BATTERY CHARGER

A LIGHT DIMMER

A STAIRWAY WITH ONE LIGHT A
SWITCH AT EACH END

MAKE YOUR OWN!