



Circuit Game

(FOR BOTH Math & Science classes!)


Using the CIRCUIT SYMBOLS below as a ***DECODER SHEET***,
figure out the circuits on the ***CODE SHEET***.

DECODER SHEET


CIRCUIT SYMBOLS

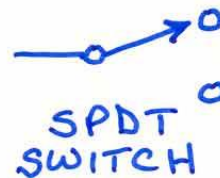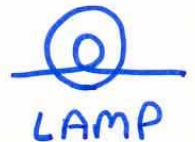


CODE SHEET

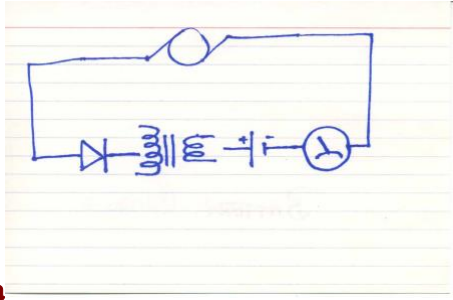


a

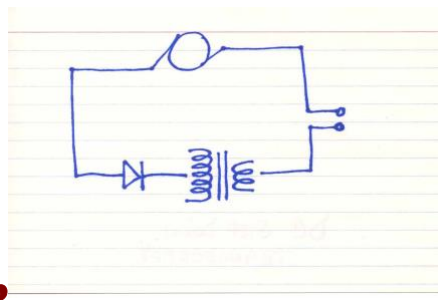


b

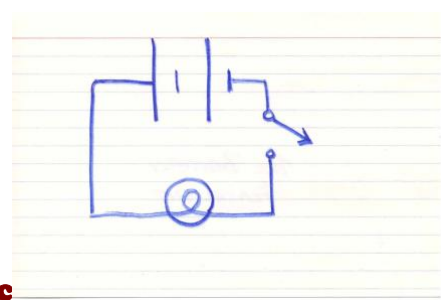


c

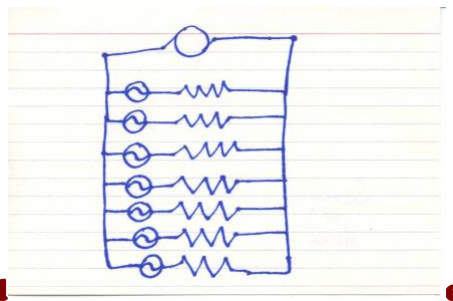


d

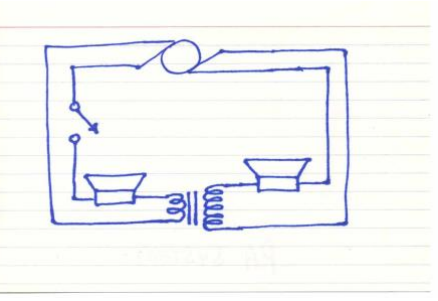


e

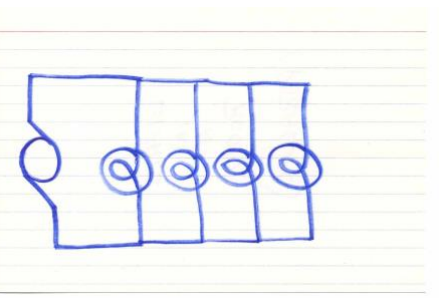


f

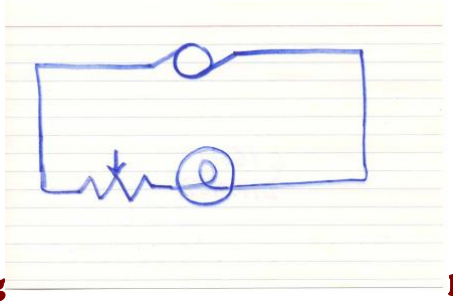


g

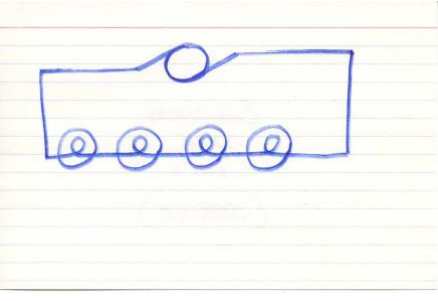


h

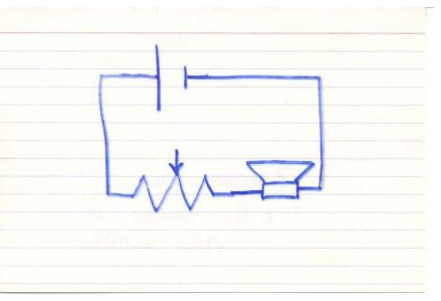

i

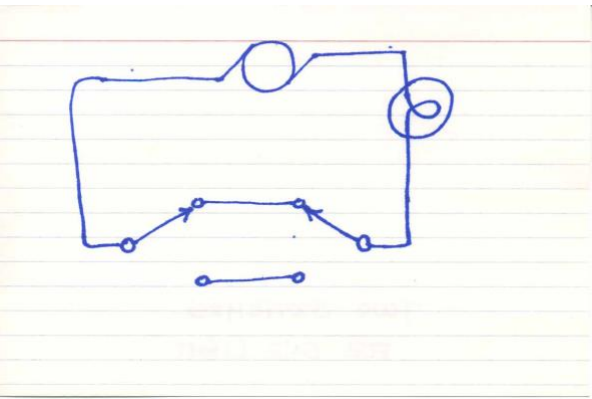

j

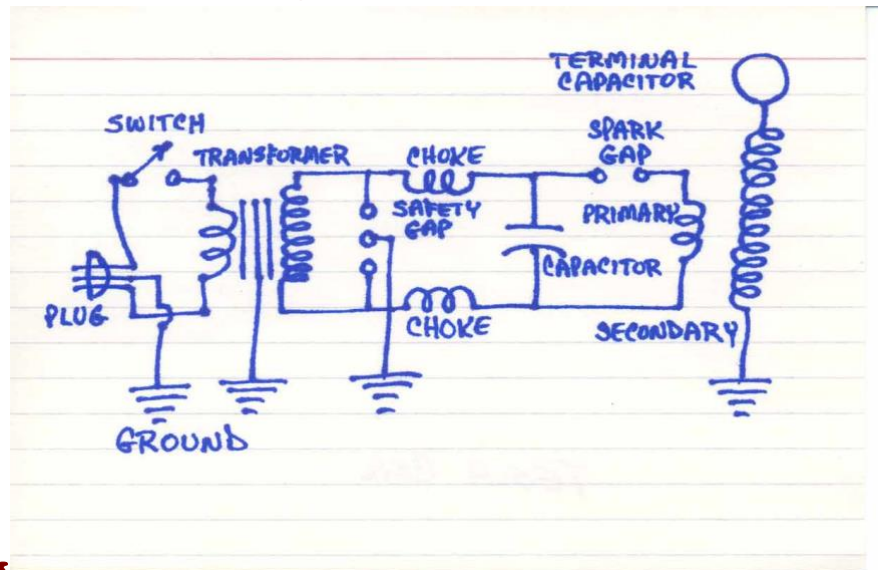

k

___ a room with lights ___ a music device ___ a DC transformer ___ a Tesla Coil ___ a few Christmas Tree lights ___ a battery charger ___ a light dimmer ___ a microphone & loud speaker ___ a flashlight ___ two switches for one light ___ a circuit breaker panel